

Sub-project 1: Design a CS amplifier with CSL

Name: Ho Wei Hao

Matric Number: A0240152X

Directory: /class2/ug24/a240152x/EE3408C_pdk180nm/Assignment/ Sub#2dProject_1

Introduction (background and objectives)

This project is focused on designing a sing-stage Common Source amplifier with CSL. This amplifier must follow the specifications detailed below.

- Supply voltage (V_{DD}) of 1.8 V
- Open-loop DC Gain: $> 40\text{dB}$
- Output voltage swing: $> 1.0\text{ V}_{p-p}$
- DC output voltage: $\sim 0.9\text{ V}$
- Total current: $< 0.4\text{ mA}$
- Maximum channel width: $500\text{ }\mu\text{m}$

The circuit layout is detailed below:

 


Figure 1. Template circuit provided

It is understood that the amplification is performed by M1. M2, along with the mirror current, helps to set the drain current which flows through M1. With this understanding, the two halves of the circuit is considered separately.

Circuit design with necessary hand calculations

First, both M1 and M2 MOSFETS must operate in saturation mode to operate as an amplifier.

Given the specifications, V_{output} is expected to swing between 0.4V to 1.4V at least. Hence, the maximum overdrive voltage for M1 and M2 to be 0.4V. We will assume 0.2V as the overdrive voltage.

Along with the value of V_{OD} , we also assume the DC component of V_{output} is 0.9V, and the drain current of M1 and M2 is $25\mu\text{A}$.

For M1,

$$V_{OD} > V_{SG} - |V_{THP}|$$

$$V_{SG} < 0.2 + 0.45$$

$$V_{SG} < 0.65\text{V}$$

$$1.8 - V_G < 0.65\text{V}$$

$$V_G > 1.15\text{V}$$

Similarly, for M2,

Sub-project 1: Design a CS amplifier with CSL

$$V_{OD} > V_{GS} - V_{THN}$$

$$V_{GS} < 0.2 + 0.32$$

$$V_{GS} < 0.52V$$

$$V_G - 0 < 0.52V$$

$$V_G < 0.52V$$

Hence, 1.2V and 0.5V are applied to the gates of M1 and M2 respectively to bias both MOSFETs to operate in saturation mode.

Next, we calculate the ratio of the sizing of M2 MOSFET. This is calculated using the drain current equation.

$$I_D = 0.5 * k_n * (W/L)_n * (V_{GS} - V_{THN})^2 * (1 + \lambda * V_{DS})$$

$$\text{With } k_n = 4.9 * 10^{-5}, I_D = 25\mu A, V_{GS} = 0.6V$$

$$(W/L)_n = 30.399... = 30.4 \text{ (3 s.f.)}$$

The sizing ratio of M1 MOSFET is calculated using the g_m equations.

$$V_{OD} = 2 * I_D / g_m$$

$$g_m = 2 * I_D / V_{OD}$$

$$g_m = (2 * 25 * 10^{-6}) / (0.6 - 0.45) = 2 * 10^{-4}$$

Using relationship $g_m = 2 * I_D / V_{OD}$

$$g_m = 2 * I_D / V_{OD} = 2 * (0.5 * k_p * (W/L)_p * V_{OD}^2) / V_{OD} = k_p * (W/L)_p * V_{OD}$$

$$(W/L)_p = 2 * 10^{-4} / (3.6 * 10^{-5}) / (0.5 - 0.32)$$

$$= 30.864... = 30.9 \text{ (3 s.f.)}$$

After obtaining these ratios, arbitrary values of width and length of the MOSFETs are calculated, starting from length L of 1u for both. The amplifier is first constructed in Cadence Spectre software without the current mirror components. The calculated sizing of the MOSFETs were inputted and tuned one variable at a time to obtain a DC output voltage of round 0.9V, and a peak-to-peak voltage of more than 1V.

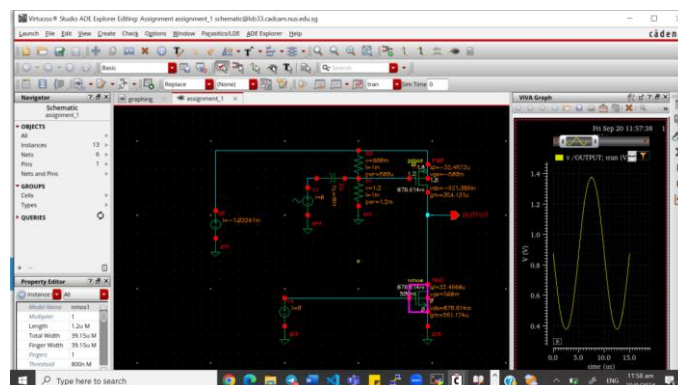


Figure 2. Amplifier circuit was constructed first, and fine-tuned later

After finetuning the MOSFETS, the actual drain current of M1 and M2 were noted down to calculate for the resistance on the current mirror side of the circuit.

From the simulation, the actual drain current is 32.4668uA, slightly higher than that assumed. Since M2 and M3 forms a current mirror, we take M2 and M3 to have the same sizing.

Sub-project 1: Design a CS amplifier with CSL

$$R_{B1} = (1.8 - 0.5) / (32.4668 \cdot 10^{-6}) = 40040.90 \dots \Omega$$

After this, the full circuit is constructed, and further fine-tuning is conducted to meet the requirements.

Cadence Spectre simulation results

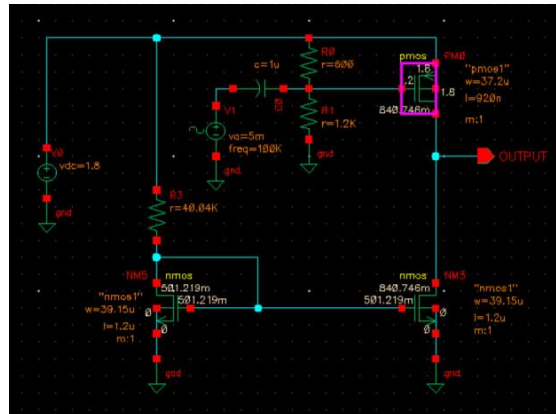


Figure 3. Final circuit with component parameters.

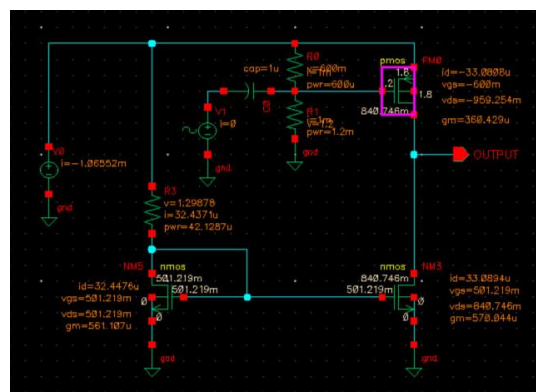


Figure 4. Final circuit with DC operating point

The transient behaviour is observed when an AC signal with amplitude 0.5mV and frequency of 100kHz is provided.

 


Figure 5. Plot of V_{output}

Sub-project 1: Design a CS amplifier with CSL

Observations

From tuning the amplifier, a series of observations can be made. Generally, increasing the width of M1 may increase or decrease the gain of the amplifier at times. This is because the transconductance of M1 is directly proportional to g_m , which in turn is directly proportional to A_v through $A_v = g_m * r_{out}$. However, increasing the width of M1 also decreases the output resistance of M1, which reduced A_v too. The overall increase or decrease in gain is dependent on the other parameters.

Similarly, if the length of M1 is increased, the DC component of V_{output} decreases, while increasing the length of M2 will increase the DC component of V_{output} . This is because the output resistance of the transistors is directly proportional to its length, which results in greater voltage drop across the V_{DS} of the transistor whenever its length is increased.

Increasing the width of M2 decreases drain current of M1, hence resulting in a smaller voltage drop across V_{DS} of M2, leading to decreasing DC component of V_{output} .

Discussions of results and observations

From Figure 5, the output swings from 0.34123V to 1.34866V, providing a peak-to-peak voltage swing of 1.00743V. Since the input AC signal has an amplitude of 5mV,

$$\text{Gain} = 20 * \lg(1.00743 - (5 * 10^{-3} * 2)) = 40.064... = 40.0\text{dB} \text{ (3 s.f)}$$

The DC component of the V_{output} is 0.840746V, very close to the required 0.9V.

The current drain of M3 is 32.4476 μ A and that of both M1 and M2 is 33.0894 μ A.

$$\text{Total current flow} = 32.4476 + 33.0894 = 65.537\mu\text{A} < 0.4\text{mA}$$

The maximum channel width of the MOSFETs did not exceed the 500 μ m limit.

Conclusion

In this project, a Common Source amplifier with current source load has been successfully designed to meet the required specifications. The key results of the design include:

- Gain of slightly larger than 40dB
- DC output voltage of 0.840746V
- Peak-to-peak voltage swing of 1.00743V

The circuit was split into two parts for consideration, on the right consisting of the amplifier circuit, and the current mirror on the left. Considering the amplifier circuit first, hand calculations provided rough values to simulate the amplifier's performance. Further tweaking is required due to unaccounted issues during calculations.

After the first iteration of tweaking, the DC operating point and the resultant drain current through M1 and M2 were noted. From this data, the resistance of the resistor on the current mirror is then calculated, and the rest of the circuit is built and simulated. A second round of tuning is required to ensure that the specifications are met.

Through this project, a better understanding of the relationships of the parameter is appreciated. The workflow on tackling such design problems is also better understood over the course of the project.